

# IDP Questions Creation

Name:

Roll no:

Code : TJKZMLAZFS

Scan/click for YouTube playlist  
to learn solving these questions.




## 1 Power Systems

1. Two resistances  $R_1$  and  $R_2$  are connected in series.

What is the equivalent resistance ?

- A.  $86.00 \Omega$
- B.  $33.00 \Omega$
- C.  $53.00 \Omega$
- D.  $20.34 \Omega$

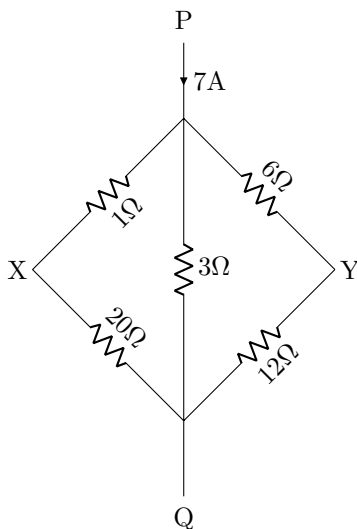2. Find the potential difference between P and Q.



- A. 0.44
- B. 2.29

C. 16.04

D. 3.06

3. A transformer has its maximum efficiency of 98% at 25 kVA at upf. During the day it is loaded as follows:

12 hours : 1 kW at pf 0.5 lag

6 hours : 6 kW at pf 0.5 lag

6 hours : 14 kW at pf 0.5 lag

Find the all day efficiency of the transformer

- A. -76.915 %
- B. 47.004 %
- C. 5.993 %
- D. 94.007 %

4. A transformer has its maximum efficiency of 98% at 26 kVA at upf. During the day it is loaded as follows:

12 hours : 4 kW at pf 0.6 lag

6 hours : 9 kW at pf 0.7 lag

6 hours : 17 kW at pf 0.4 lag

Find the all day efficiency of the transformer

- A. 5.213 %
- B. 94.787 %
- C. -50.181 %
- D. 47.394 %


5. Two resistances  $R_1$  and  $R_2$  are connected in series.

What is the equivalent resistance ?

- A.  $66.00 \Omega$
- B.  $35.00 \Omega$
- C.  $31.00 \Omega$
- D.  $16.44 \Omega$


6. A transformer has its maximum efficiency of 98% at 22 kVA at upf. During the day it is loaded as follows:  
 12 hours : 6 kW at pf 0.5 lag  
 6 hours : 8 kW at pf 0.6 lag  
 6 hours : 19 kW at pf 0.4 lag  
 Find the all day efficiency of the transformer

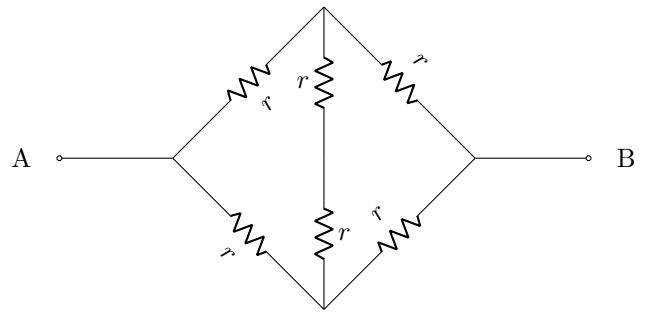- A. 5.249 %
- B. 94.751 %
- C. 47.376 %
- D. -36.443 %



- A. 0.005  $\Omega$
- B. 182.000  $\Omega$
- C. 364.000  $\Omega$
- D. 728.000  $\Omega$

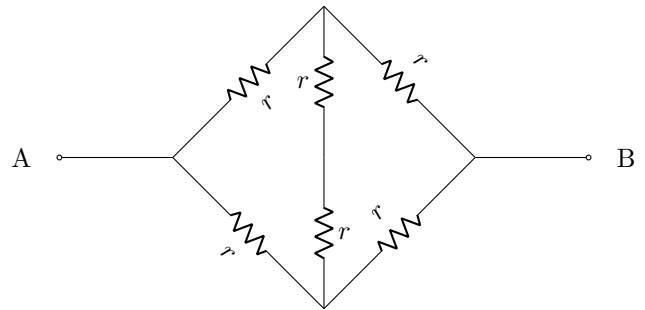9. Find the equivalent resistance between the points A and B for  $r = 443 \Omega$



- A. 0.002  $\Omega$
- B. 1772.000  $\Omega$
- C. 886.000  $\Omega$
- D. 443.000  $\Omega$

7. What will be the current density of metal if a current of 46A is passed through a cross-sectional area of  $0.1m^2$ ?

- A. 0.0022 A/ $m^2$
- B. 46000.0000 A/ $m^2$
- C. 460.0000 A/ $m^2$
- D. 4.6000 A/ $m^2$

8. Find the equivalent resistance between the points A and B for  $r = 182 \Omega$

\* \* \* All the Best \* \* \*



Scan / click the QR code to submit your answers.